

Resonance half bridge LLC converter analysis.

- ▶ Main iteration routine
- ▶ Ferrite loss calculator


Logarithmic sweep of capacitor start voltage:

Min. capacitor start voltage: $V_{cmin} \equiv 1$

Max. capacitor start voltage: $V_{cmax} \equiv 1000$

Number of steps pr. decade: $S \equiv 100$ $i \equiv 0, 1.. S \cdot \log\left(\frac{V_{cmax}}{V_{cmin}}\right)$ $V_i \equiv V_{cmin} \cdot 10^{\frac{i}{S}}$


Plot to max. power: $Pmax \equiv 500$


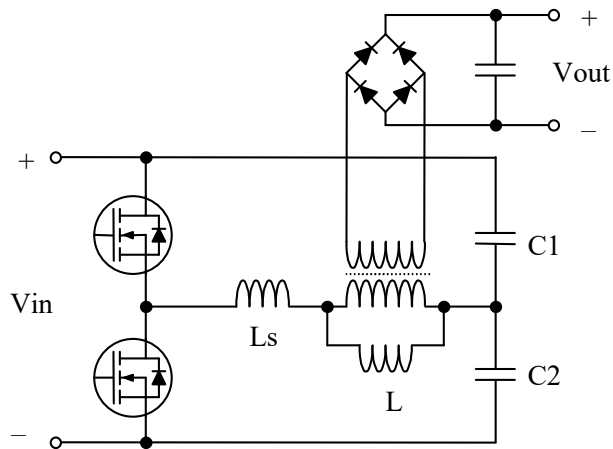


Basic half bridge resonance LLC converter.

Input voltages:
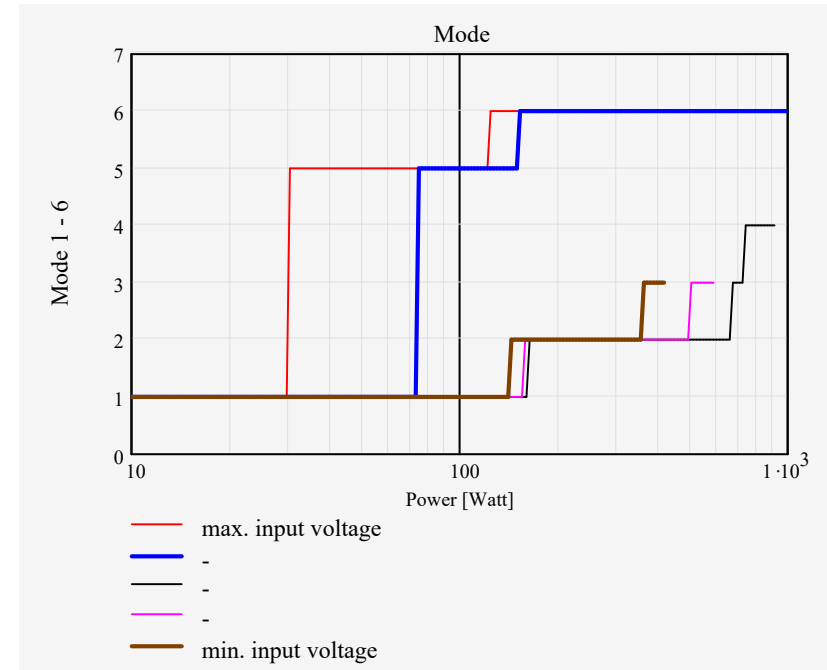
$$\begin{pmatrix} VI_4 \\ VI_3 \\ VI_2 \\ VI_1 \\ VI_0 \end{pmatrix} = \begin{pmatrix} 460 \\ 410 \\ 360 \\ 310 \\ 260 \end{pmatrix}$$



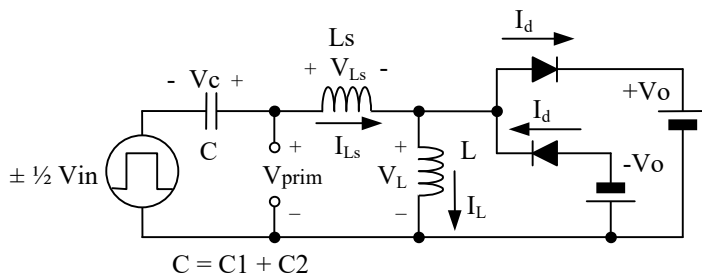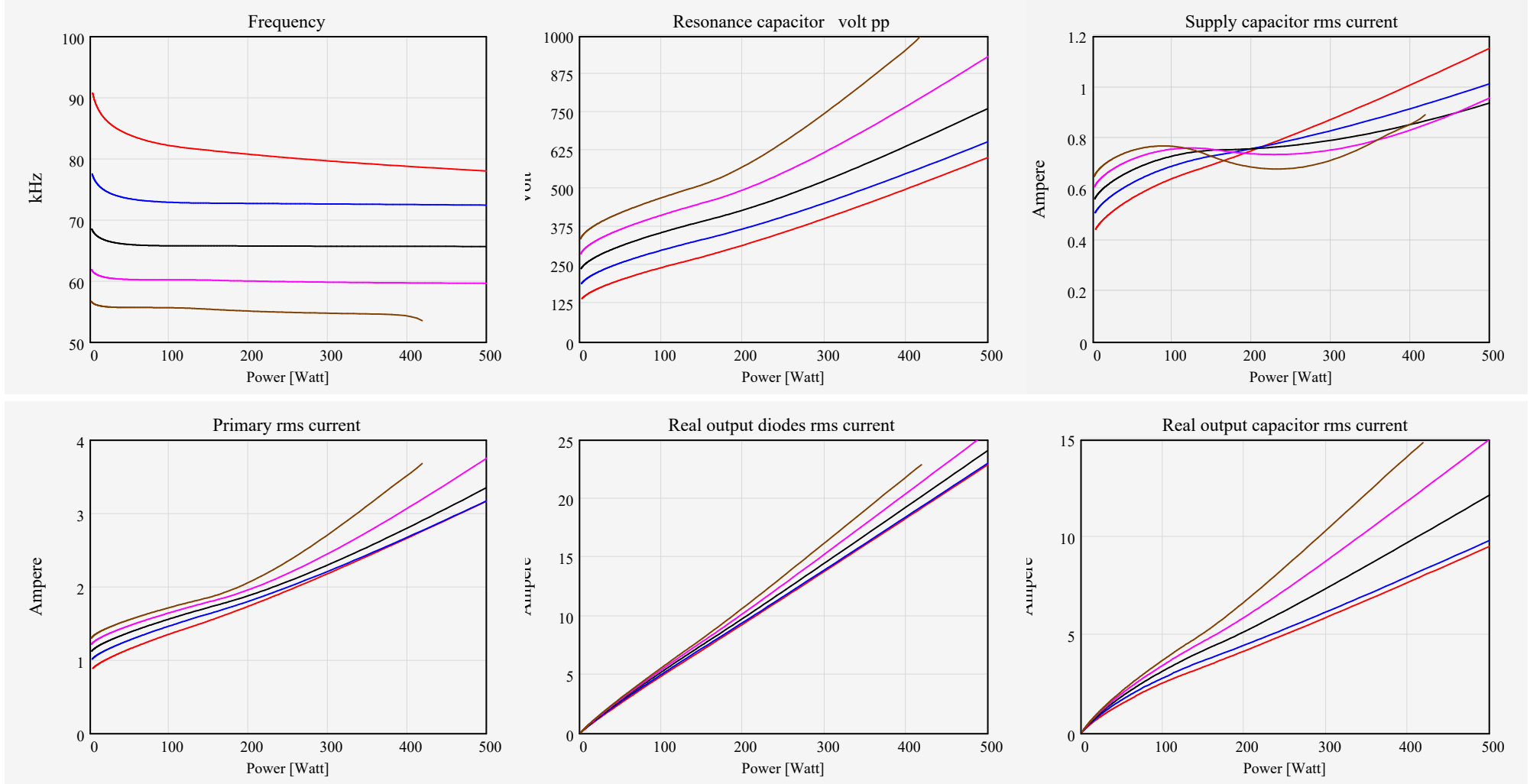

LLC converter model

Data input:

Selected component values:

Input voltage V_{in} :

Real output voltage:

Fictitious output voltage in model:

Inductance pr. turn² ratio:

$C \equiv 30 \cdot 10^{-9}$

$V_{min} \equiv 260$

$V_{out} \equiv 24$

$V_o \equiv 196$

$AL_p/AL_s \equiv 1$

$L_s \equiv 172 \cdot 10^{-6}$


$V_{max} \equiv 460$

$L \equiv 344 \cdot 10^{-6}$




Primary inductance: $L_{prim} = 516 \times 10^{-6}$

Coupling coefficient: $k = 0.816$

Turns ratio: $N_p / N_s = 10.00$

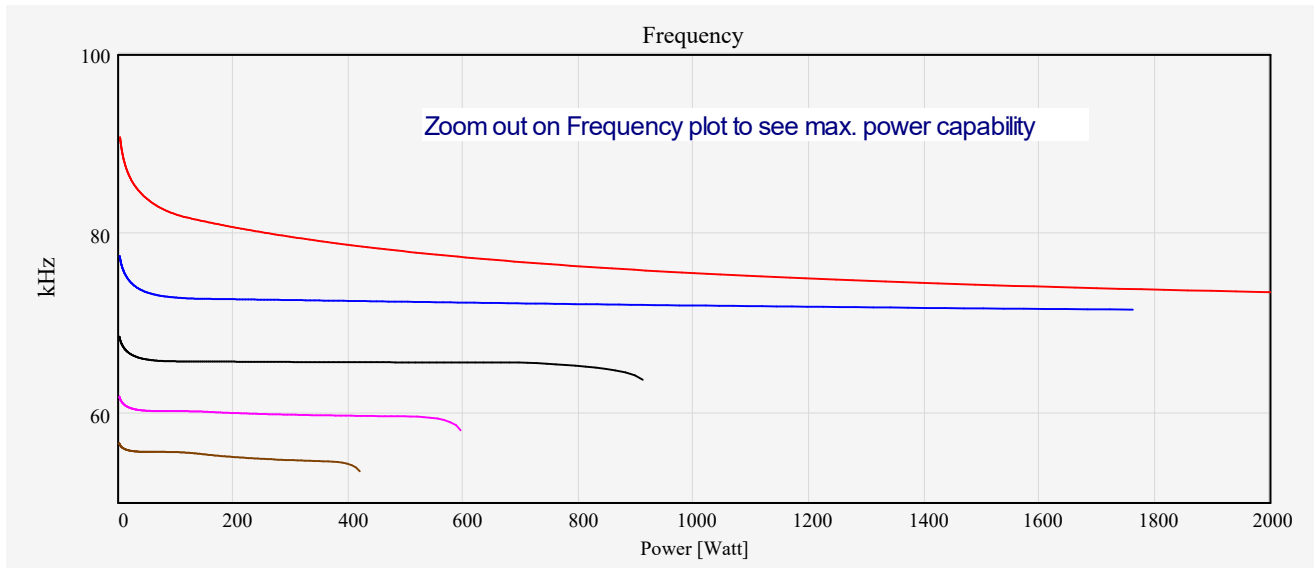
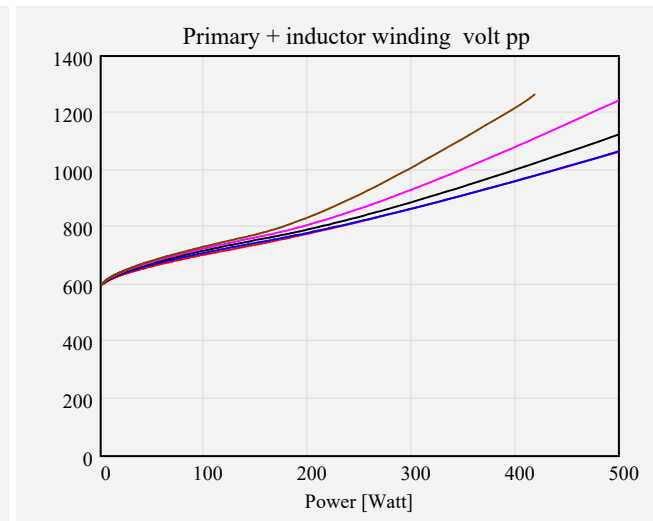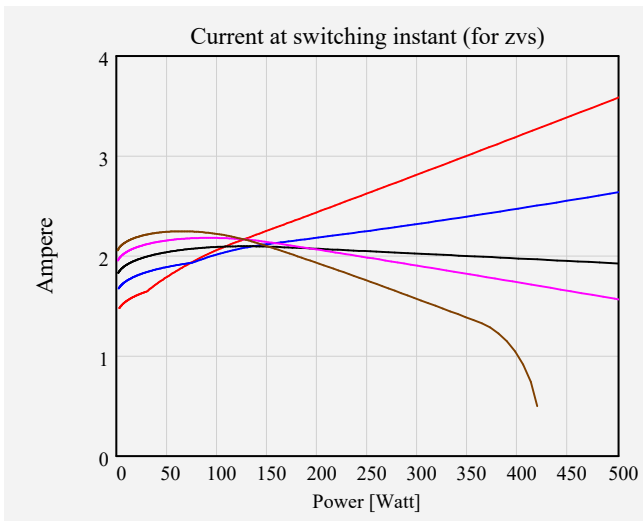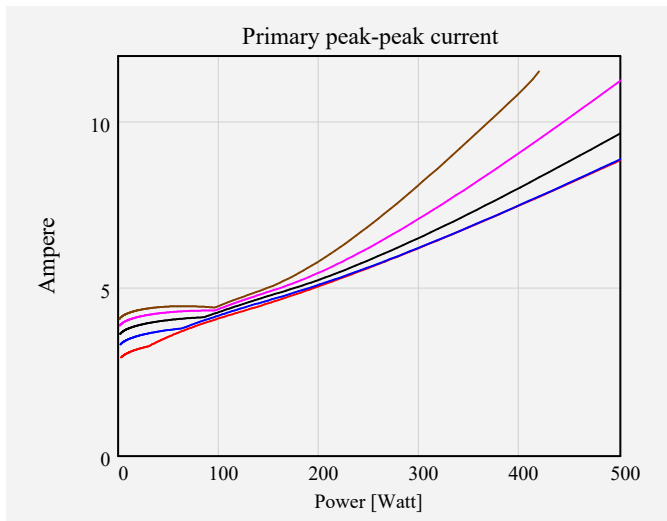
$$\begin{pmatrix} VI_4 \\ VI_3 \\ VI_2 \\ VI_1 \\ VI_0 \end{pmatrix} = \begin{pmatrix} 460 \\ 410 \\ 360 \\ 310 \\ 260 \end{pmatrix}$$



Time plots.

For check of the above results and for comparison with scope pictures or simulation, currents and voltages in the model are plotted within one switching cycle in which the input voltage starts positive.

Input voltage is switched between $-\frac{1}{2} V_{in}$ and $\frac{1}{2} V_{in}$.

Choose a capacitor start voltage V_c and an input voltage V_{in} .

Note the "Status" sign to keep an eye on problems.

Time plot data input:

Power: Power \approx 420

Input DC voltage: V_{in} \approx 261

Frequency = 54×10^3

I_{RMS} = 3.68

I_{ORMS} = 22.96

I_{LYT} = 14.87

V_{C,pp} = 1×10^3

ΔI_{LS} = 11.51

V_{out} = 24

V_o = 196

C = 30×10^{-9}

L_s = 172×10^{-6}

L = 344×10^{-6}


Approx. air gap in core [mm]: gap = 0.92

Load independent point at

Frequency: F_{lip} = 70.1×10^3 Hz

Input voltage: V_{inlip} = 392

Status = "OK"

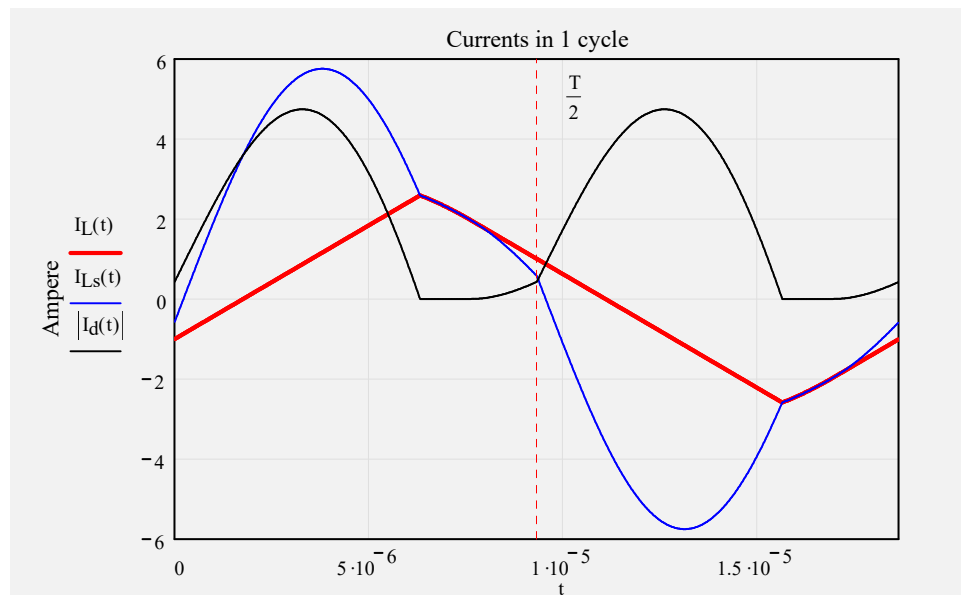


Currents and voltages in the model.

$I_L(t)$: current in magnetising inductor.

$I_{LS}(t)$: current in primary winding and switches.

$|I_d(t)|$: current in output diodes all together (in model).

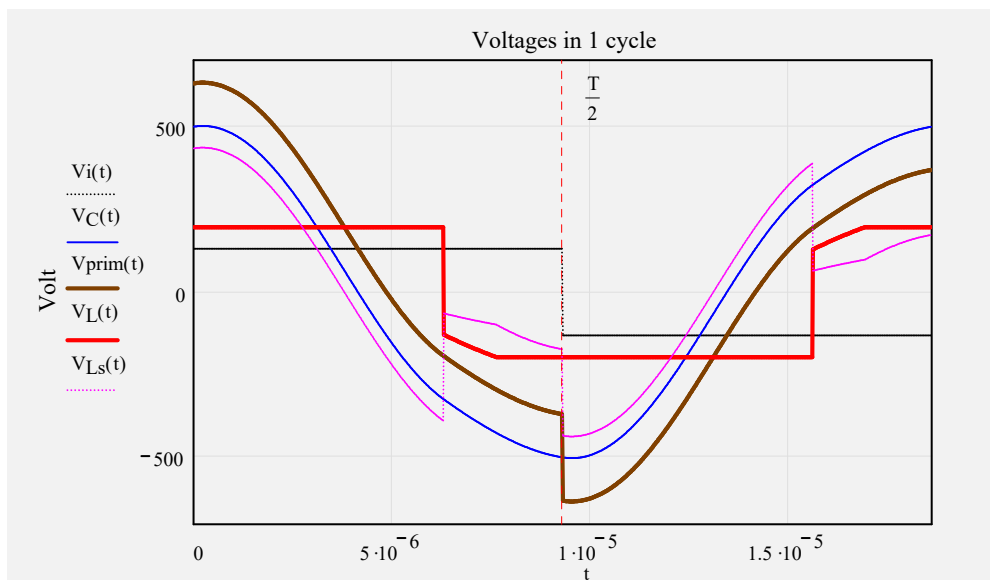

$V_i(t)$: Input square wave voltage.

$V_C(t)$: Resonance capacitor AC voltage.

$V_{prim}(t)$: Voltage on input of resonance inductor L_s.

$V_L(t)$: secondary voltage (in model).
Will be clamped to $\pm V_o$

$V_{LS}(t)$: Voltage over external inductor L_s.

Mode = 3

Transformer core and winding data input:

Core cross section: $A_{fe} \equiv 125 \cdot 10^{-6} \text{ [m}^2\text{]}$ **ETD39**
 Core volume: $vol_{fe} \equiv 11.5 \text{ [cm}^3\text{]}$
 Primary turns number: $N_p \equiv 50$
 Ferrite type: $ferrite \equiv 3$

ferrite = 1	~ 3C90
ferrite = 2	~ 3C94
ferrite = 3	~ 3C95
ferrite = 4	~ 3F3

copper resistivity @ 25°C [$\Omega \cdot \text{mm}$] $\rho_{cu} \equiv 17 \cdot 10^{-6}$

wire temperature [°C] $temp \equiv 100$
 diameter primary [mm] $\varnothing_{prim} \equiv 20$
 diameter secondary [mm] $\varnothing_{sek} \equiv 20$
 diameter primary wire [mm] $\varnothing_{primwire} \equiv 0.05$
 diameter secondary wire [mm] $\varnothing_{sekwire} \equiv 0.05$
 parallel primary wires $parprim \equiv 225$
 parallel secondary wires $parsek \equiv 1260$

If you use external inductor on input side, write **inductor = "external"**.

Otherwise Ls is integrated in the transformer:

$inductor \equiv \text{"internal"}$

Transformer turns numbers:


$N_p = 50$
 $N_s = 5.0$

Primary wire resistance:

$R_{prim} = 157 \times 10^{-3}$


Secondary wire resistance:

$R_{sek} = 2.79 \times 10^{-3}$

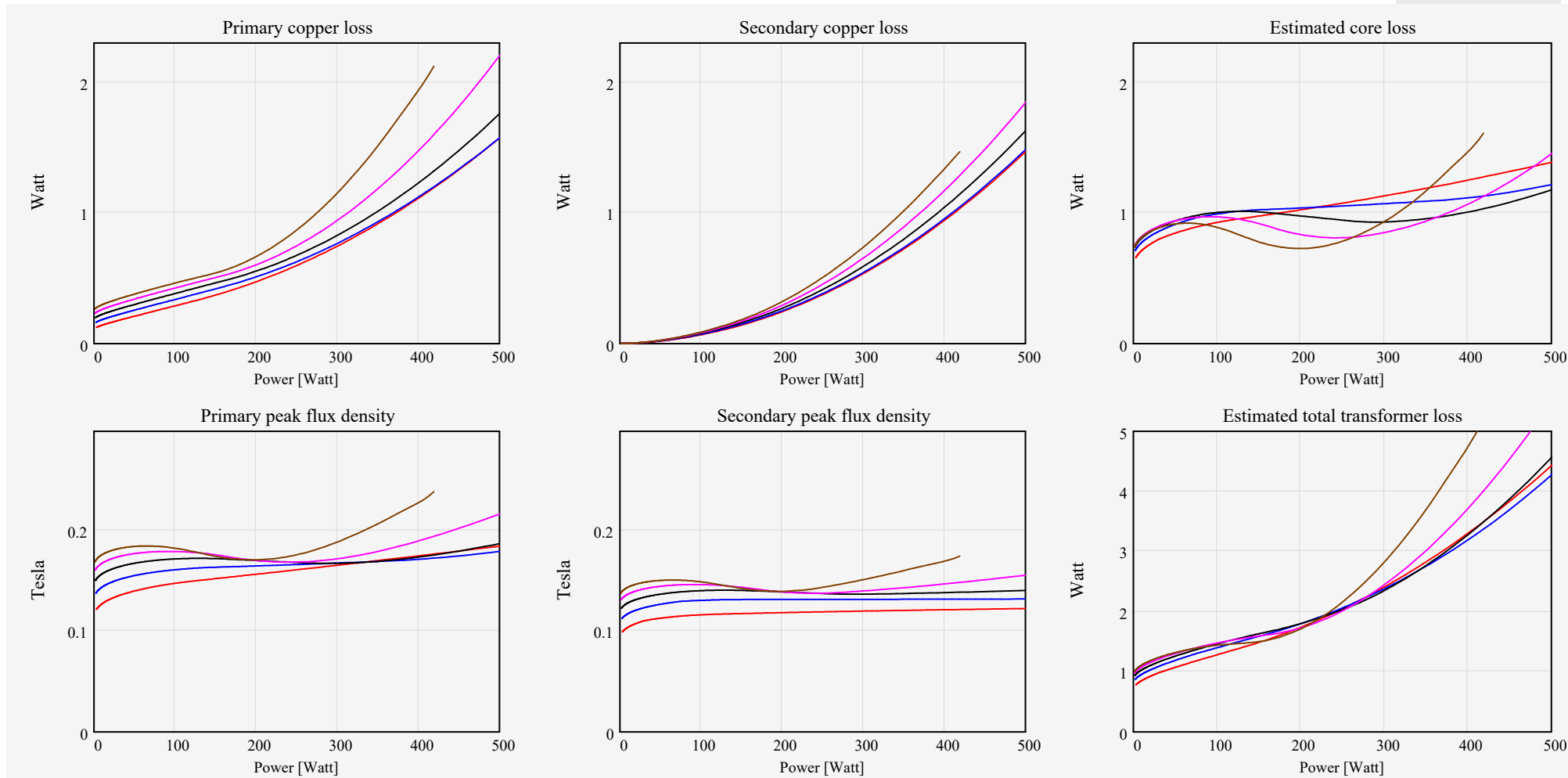

Charge mode application with L6598.

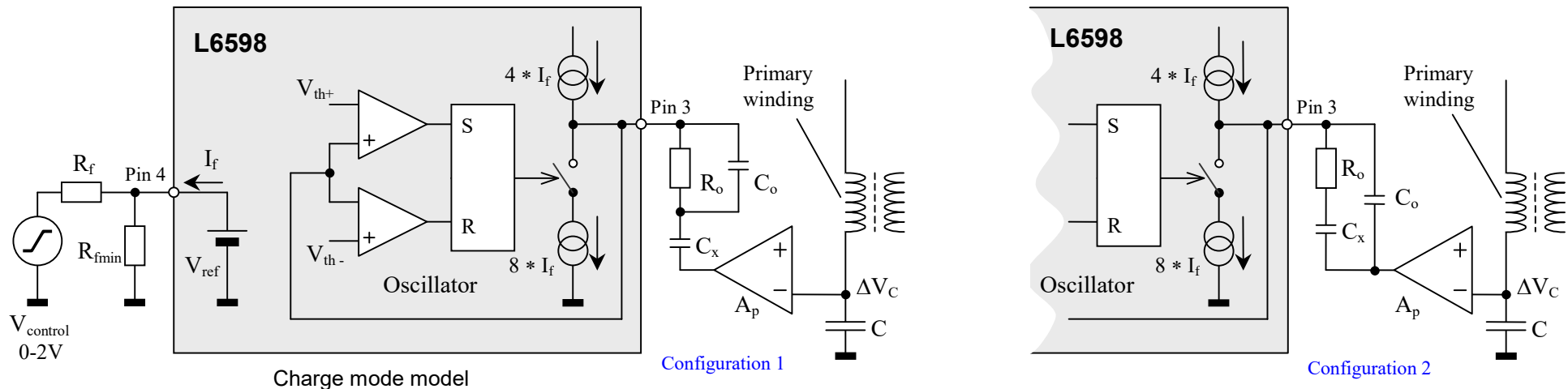
Design of control graphs for regulation loop linearity.



Charge mode equations

Control data input:

- Oscillator peak-peak voltage pin 3: $\Delta V_{th} \equiv 2.9$
- Pin 4 reference voltage: $V_{ref} \equiv 2$
- RC configuration - see above: configuration $\equiv 2$
- Oscillator capacitor: $C_o \equiv 220 \cdot 10^{-12}$
- Resistor in RC network: $R_o \equiv 6800$
- DC blocking capacitor: $C_x \equiv 1$
- Start-up resistor: $R_{fmin} \equiv 220 \cdot 10^3$
- Frequency programming resistor: $R_f \equiv 39 \cdot 10^3$
- Charge signal inverter gain: $A_p \equiv 2.3 \cdot 10^{-3}$

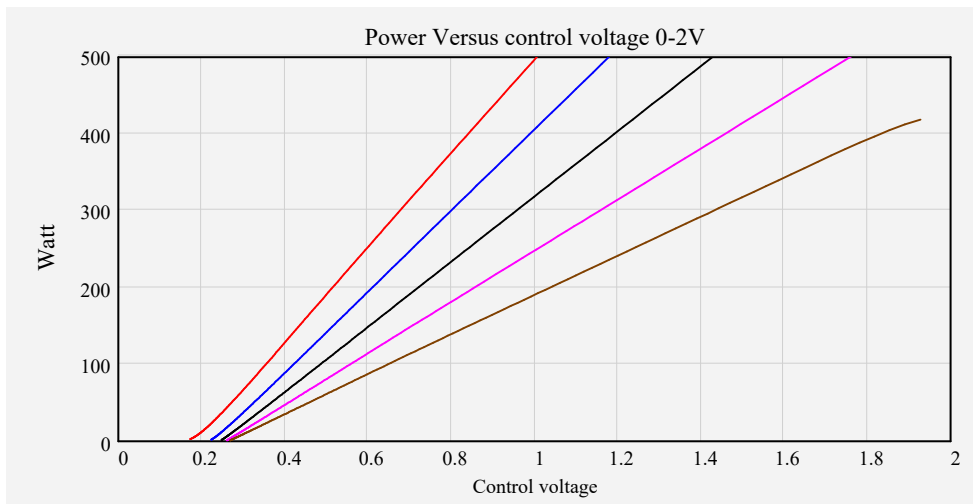

Input voltages:

$$\begin{pmatrix} VI_4 \\ VI_3 \\ VI_2 \\ VI_1 \\ VI_0 \end{pmatrix} = \begin{pmatrix} 460 \\ 410 \\ 360 \\ 310 \\ 260 \end{pmatrix}$$